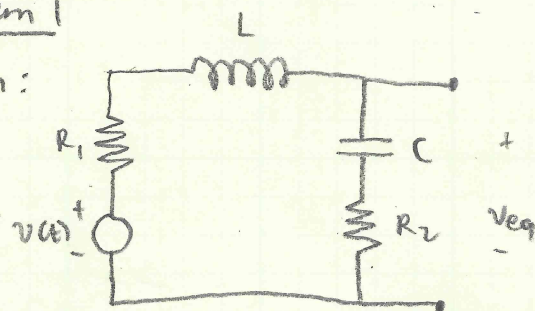
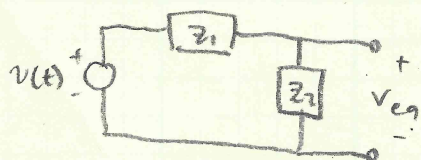


Problem 1

Given:

Find: V_{eq} and Z_{eq} 

$$Z_1 = Z_L + Z_{R_1} \\ = sL + R_1$$

$$Z_2 = Z_C + Z_{R_2} \\ = \frac{1}{sC} + R_2 \\ = \frac{sR_2C + 1}{sC}$$

$$V_{eq} = \frac{Z_2}{Z_1 + Z_2} v(t)$$

$$= \frac{\frac{sR_2C + 1}{sC}}{sL + R_1 + \frac{sR_2C + 1}{sC}} v(t)$$

$$= \frac{sR_2C + 1}{s^2LC + sR_1C + sR_2C + 1} v(t) = \frac{sR_2C + 1}{s^2LC + sC(R_1 + R_2) + 1} v(t)$$

$$V_{eq} = \frac{sR_2C + 1}{s^2LC + sC(R_1 + R_2) + 1} v(t)$$

$$Z_{eq} = Z_1 + Z_2$$

$$= sL + R_1 + \frac{sR_2C + 1}{sC}$$


$$= \frac{s^2LC + sR_1C + sR_2C + 1}{sC}$$

$$Z_{eq} = \frac{s^2LC + sC(R_1 + R_2) + 1}{sC}$$

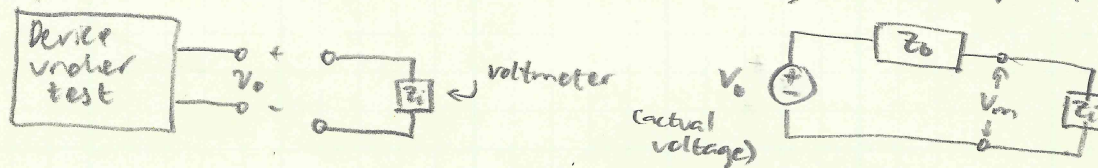Problem 2

- Why should a voltmeter have high resistance?

Ans: Below is a diagram of measuring the voltage of a device.




The transfer function of the measured voltage to the actual voltage is $G(s) = \frac{V_m}{V_0} = \frac{1}{1 + \frac{Z_0}{Z_i}}$. Since we want V_m to be as close to V_0 as possible, $G(s)$ should be close to 1. when $Z_i \gg Z_0$, $G(s) = \frac{1}{1 + \frac{Z_0}{Z_i}} = 1$.

$$Z_i = R_i$$


Therefore, the voltmeter needs higher resistance to increase its impedance.

- Why should the resistance of an ammeter should be high?

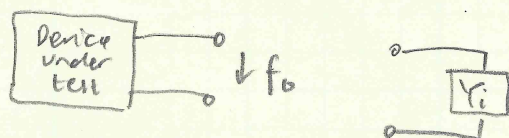Below is the diagram of measuring the current of a system.


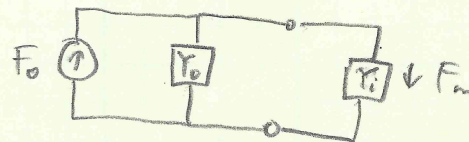
$$G(s) = \frac{I_m}{I_0} = \frac{1}{1 + \frac{Y_0}{Y_i}}$$



We want $G(s) = 1$ to accurately measure current.


when $Y_i \gg Y_0$, $G(s) = \frac{1}{1 + \frac{Y_0}{Y_i}} = 1$

$$Y_i = \frac{1}{R_i}$$

Therefore, the ammeter needs to have really low resistance to ensure that its admittance is as low as possible

Problem 3

Given:

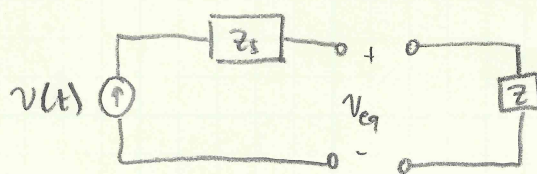Show that the power dissipated is maximum when $R = R_s$

$$P = v i$$

$$P_{\text{dissipated}} = v_{eq} \times i$$

$$v_{eq} = \frac{Z}{Z_s + Z} v = \frac{R}{R_s + R} v, \quad i = \frac{v}{R_s + R}$$

$$P_{\text{dissipated}} = \frac{R}{R_s + R} v \times \frac{v}{R_s + R} = \frac{R}{(R_s + R)^2} v^2$$


maximize $P_{\text{dissipated}}$ while changing R

$$\frac{dP(R)}{dR} = -\frac{R - R_s}{(R - R_s)^3} v^2 = 0 \leftarrow \text{maximum value}$$

$$\therefore \boxed{R = R_s} \text{ for maximum value}$$

Problem 4

Given:

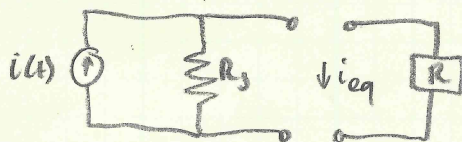Show that $P_{\text{dissipated}}$ in the resistive element is max when $R = R_s$

$$P = v i, \quad P_{\text{dissipated}} = v_{eq} \times i_{eq}$$

$$i_{eq} = \frac{Y}{Y_s + Y} i = \frac{\frac{1}{R}}{\frac{1}{R_s} + \frac{1}{R}} i = \frac{\frac{1}{R}}{\frac{R + R_s}{R_s R}} i = \frac{R_s}{R + R_s} i, \quad v = i \left(\frac{1}{R} + \frac{1}{R_s} \right)^{-1}$$

$$P_{\text{dissipated}} = \frac{R_s}{R + R_s} i \times i \times \frac{R R_s}{R + R_s} = \frac{R R_s^2}{(R + R_s)^2} i^2$$

maximize $P_{\text{dissipated}}$ while changing R

$$\frac{dP(R)}{dR} = -\frac{R_s^2 (R - R_s)}{(R + R_s)^3} = 0, \quad \therefore \boxed{R = R_s} \text{ for maximum value}$$